

Analog to Digital Converters

David Andrews

dandrews@uark.edu

Slides adapted from:

ee.nmt.edu/~rison/ee308_spr02/020306.pdf

Ume.gatech.edu/mechatronics_course/ADC_F08.pdf



What is an A/D Converter ?

- Analog signals are continuous and directly measurable.
- Digital signals are discrete and only have two states $\{0, 1\}$.
- An A/D transforms (maps) the analog continuous signal to a digital discrete form.



Practical Considerations

- How fast do we need to Sample ?
 - Signal Processing gives the answer
- What is the range of values $V_{hi} - V_{lo}$?
 - Resolution of digital representation
- What error can the system tolerate ?
 - Quantization error




How do A/D's Operate ?

- Several choices
 - We will study two:
 - Flash A/D's:
 - Fastest but most expensive
 - Practical limitations on resolution (#bits)
 - Successive Approximation
 - Slower than flash but still fast and cheaper
 - Higher resolution (#bits)
- Interestingly both built on D/A components
 - Analog Comparators, resistor trees



Sampling Rate (How fast)


A 1050 Hz signal sampled at 500 Hz

 

The 1050 Hz signal looks like a 50 Hz signal !



Sampling Rate (How fast)

 

Nyquist Rate:

Need to sample at least 2x faster than highest frequency

For (pure tone) 1050 Hz, minimum sampling rate = 2100 Hz

Rule of thumb: sample at 4x - 10x highest frequency



Quantization Error

- Resolution := #bits
- 3 bit resolution gives
 - $2^3 = 8$ quantization levels
- Assume you are sampling a signal between 5volts - 0 volts

$$\frac{5v - 0v}{8} = .625v$$



Quantization Error

Volts	Encoded	
5		
4.37	111	values between 4.37 – 5 = 111
3.75	110	values between 3.75 – 4.37 = 110
3.12	101	
2.5	100	
1.875	011	0
1.25	010	0
.625	001	0
0	000	values between 1.25 – .625 = 001
		values between .625 – 0 = 000



Quantization Error

Volts Encoded

5		
	-----	111
4.37		
	-----	110
3.75		
	-----	101
3.12		
	-----	100
2.5		
	-----	011
1.87		
	-----	010
1.25		
	-----	001
.625		
	-----	000
0		

$$\text{Error} \pm \frac{1}{2} \Delta$$

$$\frac{.625}{2} = \pm .3125\text{v}$$



Accuracy of A/D Conversion


Two ways to improve the accuracy of A/D conversion:

1. increasing the resolution which improves the accuracy in measuring the amplitude of the analog signal.
2. increasing the sampling rate which increases the maximum frequency that can be measured.




Accuracy of A/D Conversion

■ Low Accuracy

 

■ Improved

 

Meet the Comparator !


A comparator is used in many types of A/D converters.

A comparator is the simplest interface from an analog signal to a digital signal

Compares two voltage values on its two inputs

If the voltage on the + input is greater than the voltage on the - input, the output will be a logic high (1)

 If the voltage on the + input is less than the voltage on the - input, the output will be a logic low (0)



If $V_{IN} > V_{REF}$ then $V_{OUT} = V_{CC}$

If $V_{IN} < V_{REF}$ then $V_{OUT} = 0$



Flash (Parallel) A/D Converter


2-bit Analogue to Digital Converter Circuit

A flash A/D converter simplest to understand

A flash A/D converter compares an input voltage to a large number of reference voltages

An n -bit flash converter uses $2^n - 1$ comparators

 The output of the A/D converter is determined by which of the two reference voltages the input signal is between



2-bit A/D converter Output

Analogue Input Voltage (V_{IN})	Comparator Outputs				Digital Outputs	
	D ₃	D ₂	D ₁	D ₀	Q ₁	Q ₀
0 to 1 V	0	0	0	0	0	0
1 to 2 V	0	0	1	X	0	1
2 to 3 V	0	1	X	X	1	0
3 to 4 V	1	X	X	X	1	1



Flash A/D Converter

An n-bit Flash A/D converter requires $2^n - 1$ comparators

- 8-bit Flash A/D requires 255 comparators
- 12-bit Flash A/D converter would require 4,095 comparators
- Cannot integrate 4,095 comparators onto an IC The largest flash A/D converter is 8 bits

Flash A/D converters can sample at several billion samples/sec




Successive Approximation

- A successive approximation (SA) A/D converter uses an intelligent scheme to determine the input voltage
- It first tries a voltage halfway between $V_{\max}$ and $V_{\min}$. Determines if the signal is in the lower half or the upper half of the voltage range
 - If the input is in the upper half of the range, it sets the most significant bit of the output
 - If the input is in the lower half of the range, it clears the most significant bit of the output
- The first clock cycle eliminates half of the possible values
 - On the next clock cycle, the SA A/D tries a voltage in the middle of the remaining possible values
 - The second clock cycle allows the SA A/D to determine the second most significant bit of the result
 - Each successive clock cycle reduces the range another factor of two

For an n -bit SA A/D converter, takes n clock cycles to determine value



Successive Approximation

 


2 steps

- Sampling and Holding (S/H)
- Quantizing and Encoding (Q/E)




Sampling and Holding

 - Holding signal benefits the accuracy of the A/D conversion
- Minimum sampling rate should be at least twice the highest data frequency of the analog signal



Successive Approximation ADC Circuit

 

- Uses a n-bit DAC to compare DAC and original analog results.
- Uses Successive Approximation Register (SAR) supplies an approximate digital code to DAC of V_{IN} .
- Comparison changes digital output to bring it closer to the input value.
- Uses Closed-Loop Feedback Conversion



Successive Approximation Example

Example

- 10 bit ADC
- $V_{in} = 0.6$ volts (from analog device)
- $V_{ref} = 1$ volts
- Find the digital value of V_{in}

Bit	Voltage
9	.5
8	.25
7	.125
6	.0625
5	.03125
4	.015625
3	.0078125
2	.00390625
1	.001952125
0	.0009765625

$N = 2^n$ (N of possible states)

$N = 1024$

$V_{max} - V_{min} / N = 1 \text{ Volt} / 1024 =$
 $0.0009765625V$ of V_{ref} (resolution)



Successive Approximation

- MSB (bit 9)
 - Divided V_{ref} by 2
 - Compare $V_{ref}/2$ with V_{in}
 - If V_{in} is greater than $V_{ref}/2$, turn MSB on (1)
 - If V_{in} is less than $V_{ref}/2$, turn MSB off (0)
 - $V_{in} = 0.6V$ and $V = 0.5$
 - Since $V_{in} > V$, MSB = 1 (on)

Bit	Voltage
9	.5
8	.25
7	.125
6	.0625
5	.03125
4	.015625
3	.0078125
2	.00390625
1	.001953125
0	.0009765625

1									
---	--	--	--	--	--	--	--	--	--



Successive Approximation

- Next Calculate MSB-1 (bit 8)
 - Compare $V_{in}=0.6\text{ V}$ to $V=V_{ref}/2 + V_{ref}/4= 0.5+0.25 =0.75\text{V}$
 - Since $0.6<0.75$, MSB is turned off
- Calculate MSB-2 (bit 7)
 - Go back to the last voltage that caused it to be turned on (Bit 9) and add it to $V_{ref}/8$, and compare with V_{in}
 - Compare V_{in} with $(0.5+V_{ref}/8)=0.625$
 - Since $0.6<0.625$, MSB is turned off

1	0	0							
---	---	---	--	--	--	--	--	--	--



Successive Approximation

- Calculate the state of MSB-3 (bit 6)
 - Go to the last bit that caused it to be turned on (In this case MSB-1) and add it to $V_{\text{ref}}/16$, and compare it to V_{in}
 - Compare V_{in} to $V = 0.5 + V_{\text{ref}}/16 = 0.5625$
 - Since $0.6 > 0.5625$, MSB-3=1 (turned on)

MSB	MSB-1	MSB-2	MSB-3	...					
1	0	0	1						



Successive Approximation ADC

- This process continues for all the remaining bits.

•Digital Results:

MSB	MSB-1	MSB-2	MSB-3	...					LSB
1	0	0	1	1	0	0	1	1	0

•Results: $\frac{1}{2} + \frac{1}{16} + \frac{1}{32} + \frac{1}{256} + \frac{1}{512} = .599609375 \text{ V}$

